

Assessment B-1

Q1

Consider a 2kW, MOSFET half-bridge converter powered from a $230V_{\text{RMS}}$ ac-source. A center-tapped secondary winding is used.

Draw a circuit diagram of the converter showing all the components required as well as the drivers. Pay special attention to the reference potentials of the drivers and output voltage. [3]

Q2

M/C

Consider a 2kW, MOSFET half-bridge converter powered from a $230V_{\text{RMS}}$ ac-source. A center-tapped secondary winding is used.

You have a large number of $1000\ \mu\text{F}$ (250V) electrolytic capacitors in stock and the total bus capacitance needs to be equal to or slightly higher than $2500\ \mu\text{F}$. How many of the capacitors will you need? [3]

Q3

Consider a 100W center-tap converter, fed from a 24V supply.

Draw a circuit diagram of the converter. [3]

Q4

M/C

Consider a 100W center-tap converter, fed from a 24 V supply and the output voltage is 300 V. The transformer efficiency is 85% but all other components may be assumed to be ideal.

The converter rectifier diodes should be rated at a minimum of: [3]

Q5

A maximum power point tracker (MPPT) comprises of an 18V, 95 W (power output capability) solar panel with an efficiency of 30%, a buck converter with an efficiency of 85% and a buck-boost converter with an efficiency of 80%. The load voltage should be maintained at 12 V, 50 W all the time.

Draw a block diagram of the system indicating the efficiencies of each of the subsystems on it. [3]

Q6

A maximum power point tracker (MPPT) comprises of a 12V, 95 W solar panel with an efficiency of 30%, a buck converter with an efficiency of 85% and a buck-boost converter with an efficiency of 80%. The load voltage should be maintained at 12 V, 50 W all the time.

The maximum power point (not necessarily 95W) operation of the panel is achieved at a specific point in time where the buck converter output is 7V. Calculate the current produced by the buck converter. [5]

Q7

A diode and MOSFET are mounted on the same heatsink. The diode dissipates 5 W and the MOSFET dissipates 10 W under specific operating conditions. The diode has a junction to case thermal resistance of 0.2 K/W and the MOSFET has a junction to case thermal resistance of 0.4 K/W. Both of them have case to sink thermal resistances of 1 K/W and the heatsink thermal resistance is 0.8 K/W. The ambient temperature is 35°C.

Draw an equivalent circuit with all the given information of the thermal problem. [3]

Q8

A diode and MOSFET are mounted on the same heatsink. The diode dissipates 5 W and the MOSFET dissipates 10 W under specific operating conditions. The diode has a junction to case thermal resistance of 0.2 K/W and the MOSFET has a junction to case thermal resistance of 0.4 K/W. Both of them have case to sink thermal resistances of 1 K/W and the heatsink thermal resistance is 0.8 K/W. The ambient temperature is 35°C.

Calculate the junction temperature of the MOSFET. Present your answer in degrees Celcius to two decimals. [5]

Q9

The efficiency of a 12 V output, buck converter is equal to 84 % at 50W output power. The input voltage varies from 15 V to 18 V. Calculate the difference in percentage duty cycle which will maintain the output voltage at 12 V. [2]